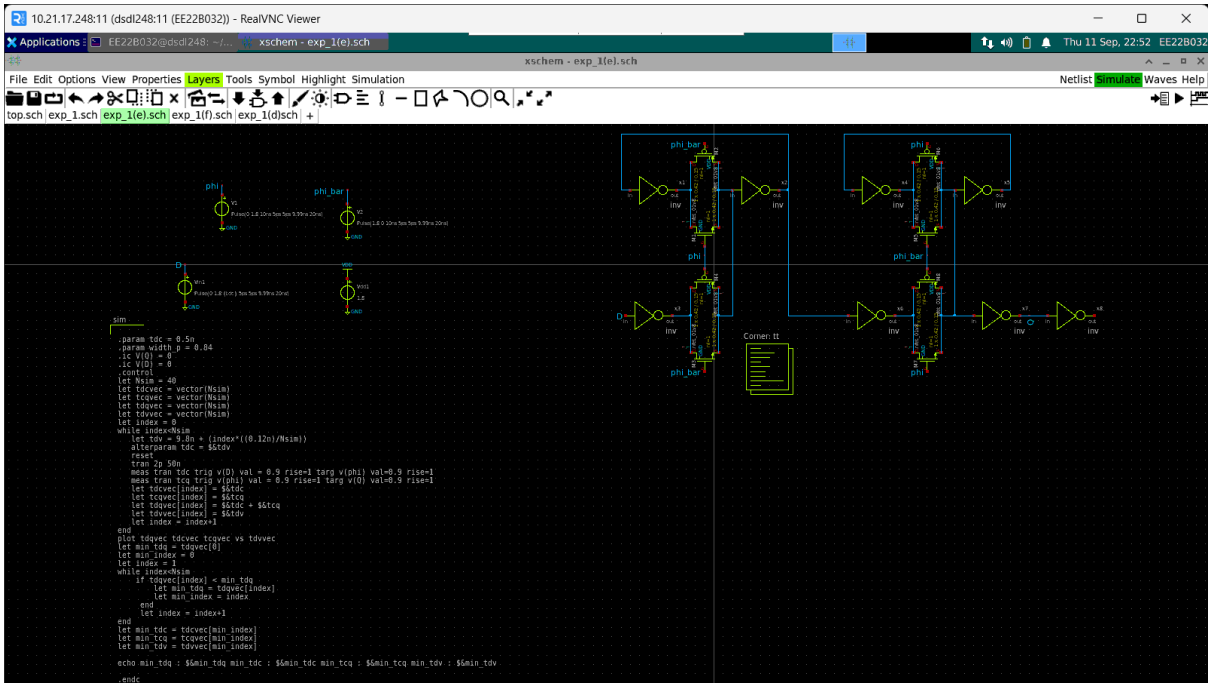
# EE5311: Digital IC Design
# Tutorial 5 Report

Putta Shravya
Roll Number: EE22B032

September 11, 2025

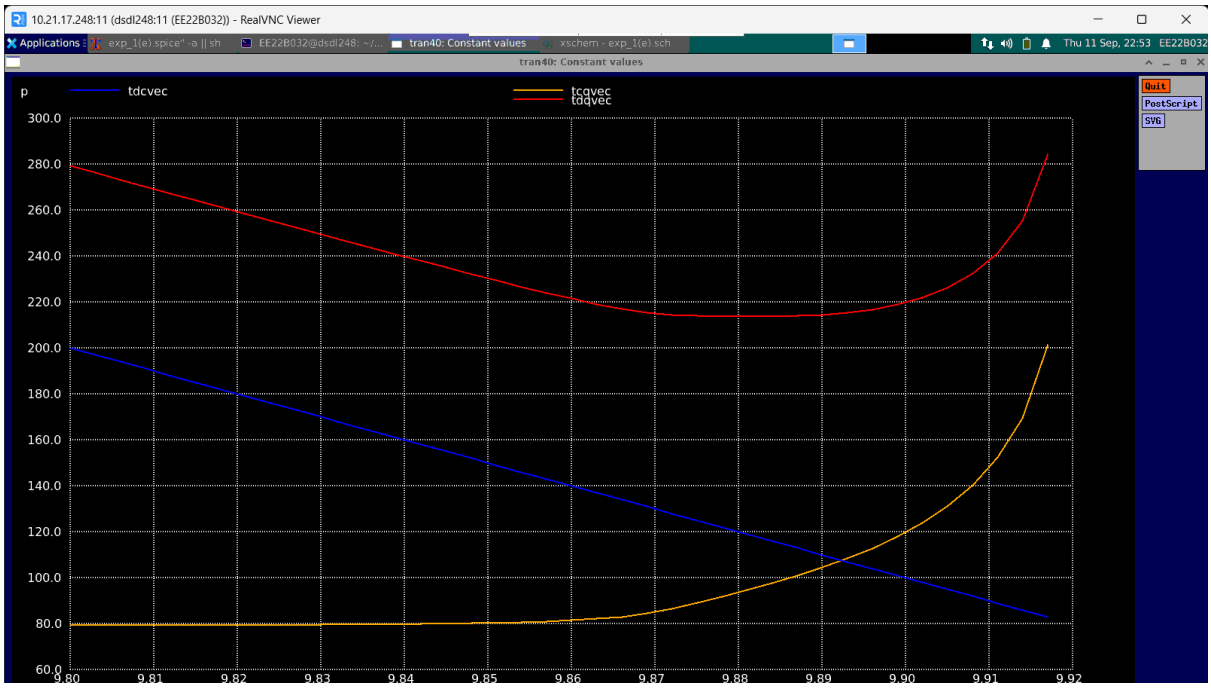
## Question 1

### Part A



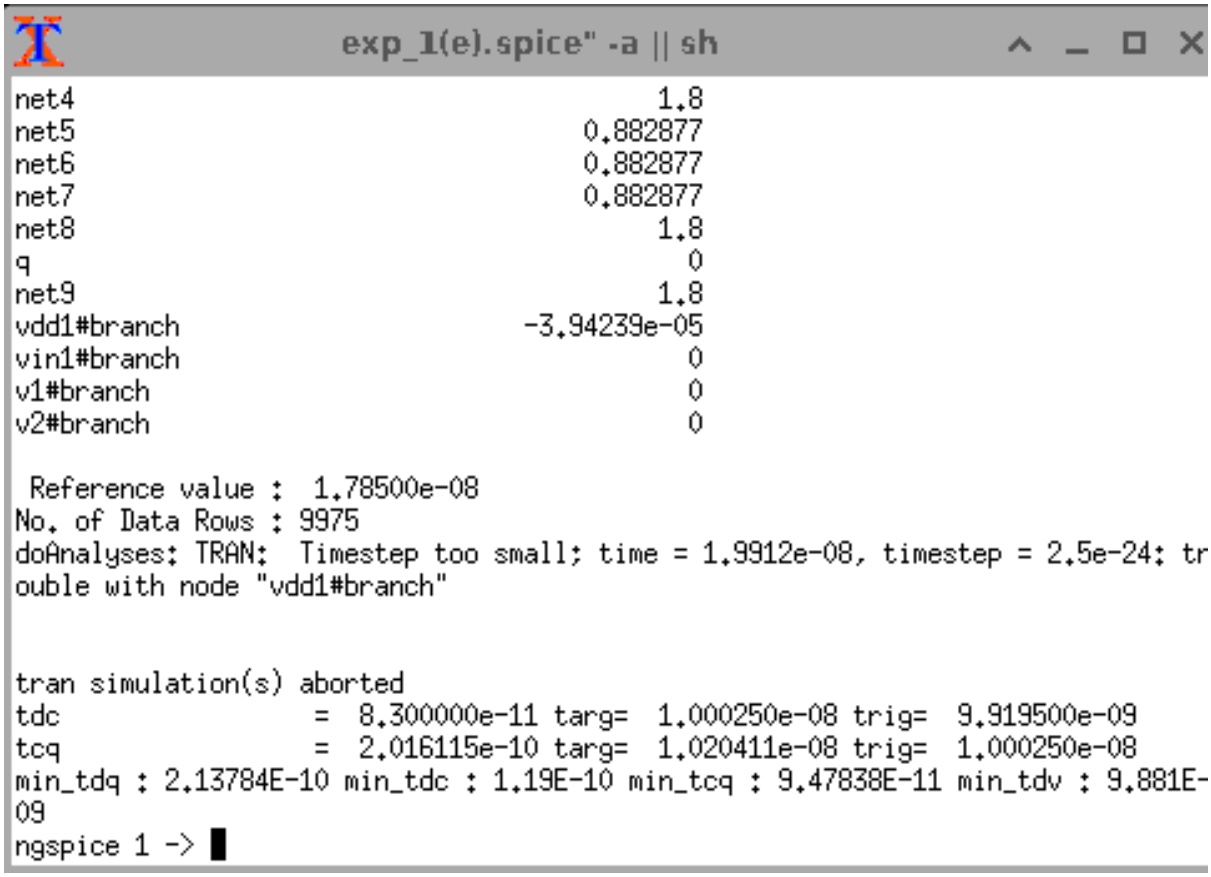

Schematic

## Plots



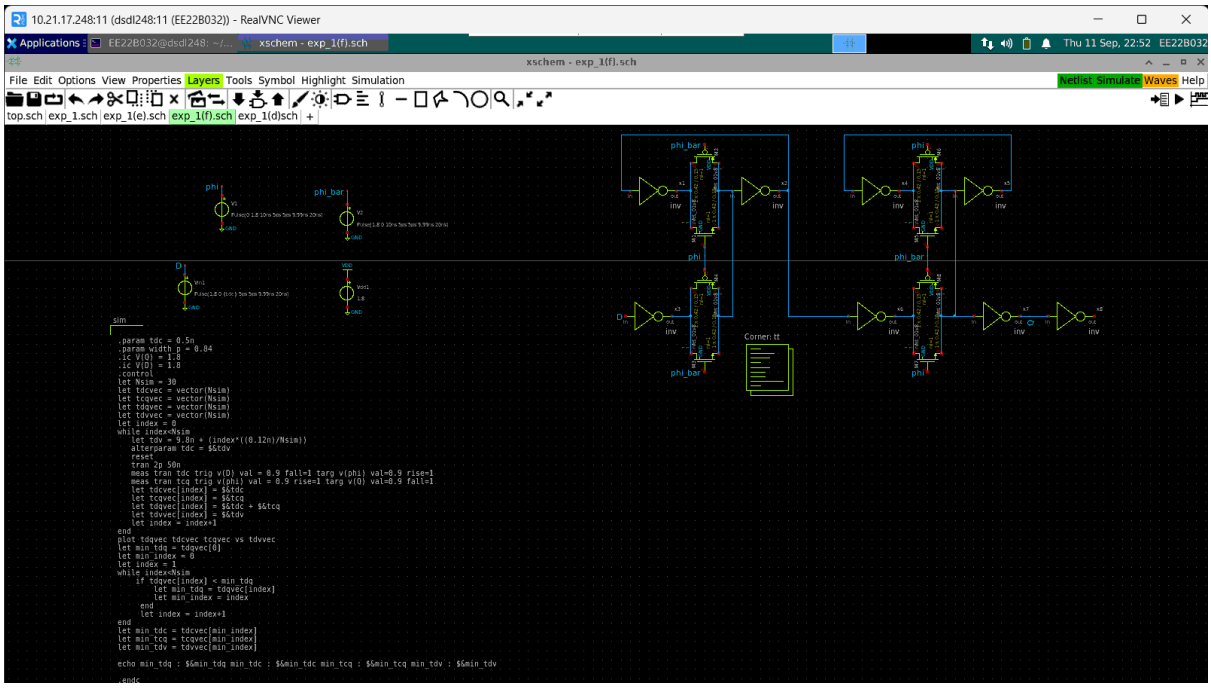

Graphs

**setup and delay time**



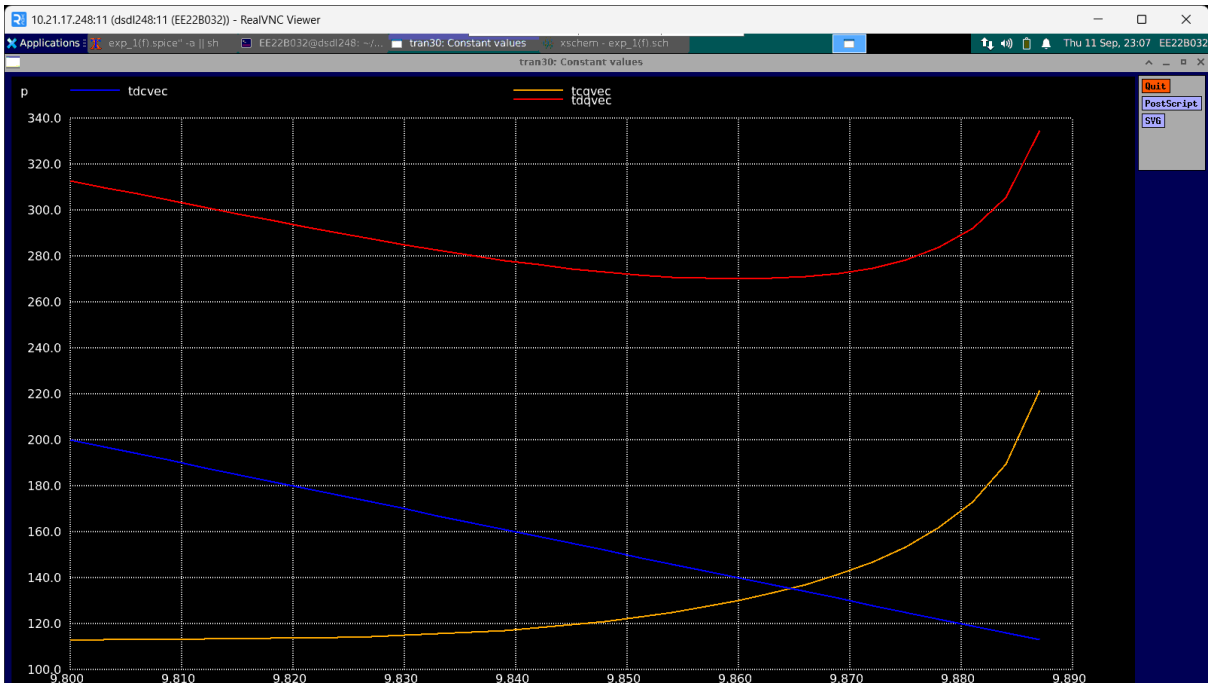

values

# Part B



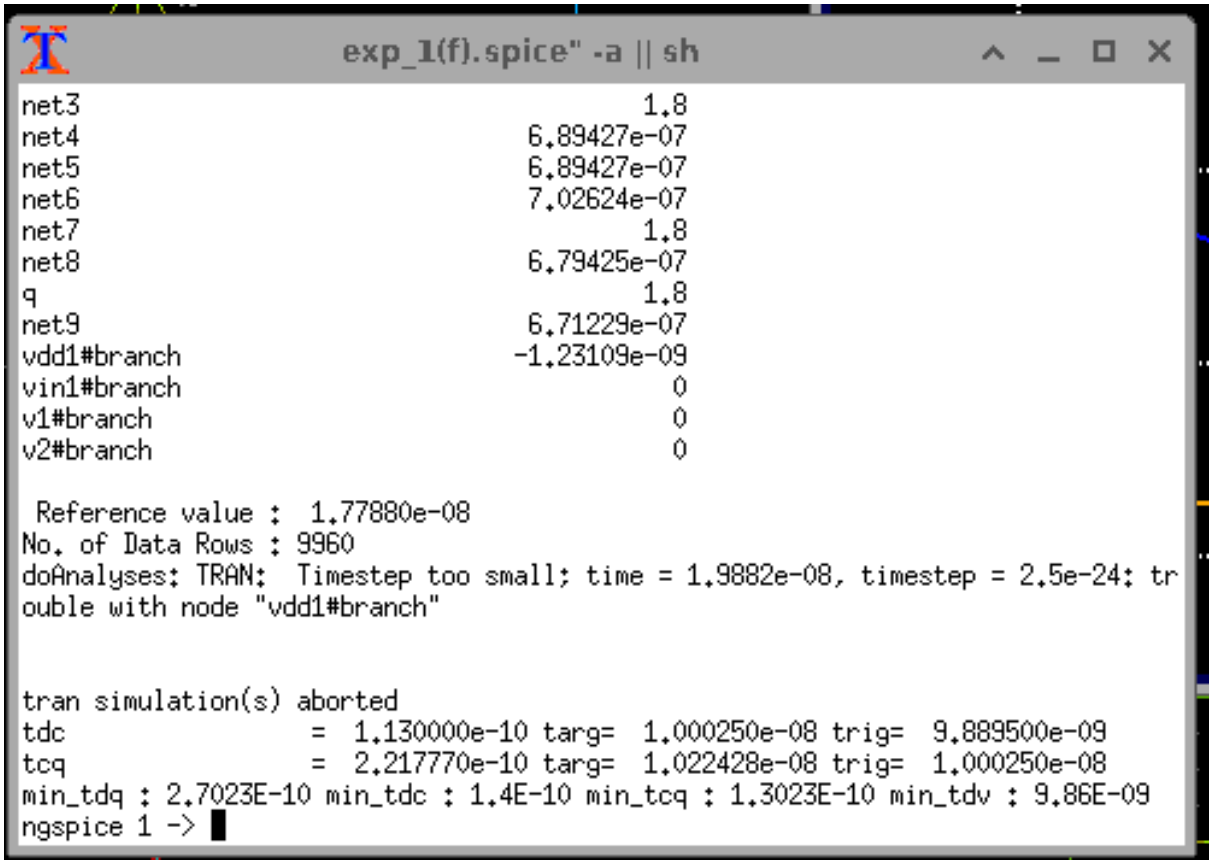

Schematic

## Plots




Graphs

**setup and delay time**




values