EE5311: Digital IC Design
Tutorial Report

Putta Shravya
Roll Number: EE22B032


October 5, 2025

Question 1

Part A




Schematic

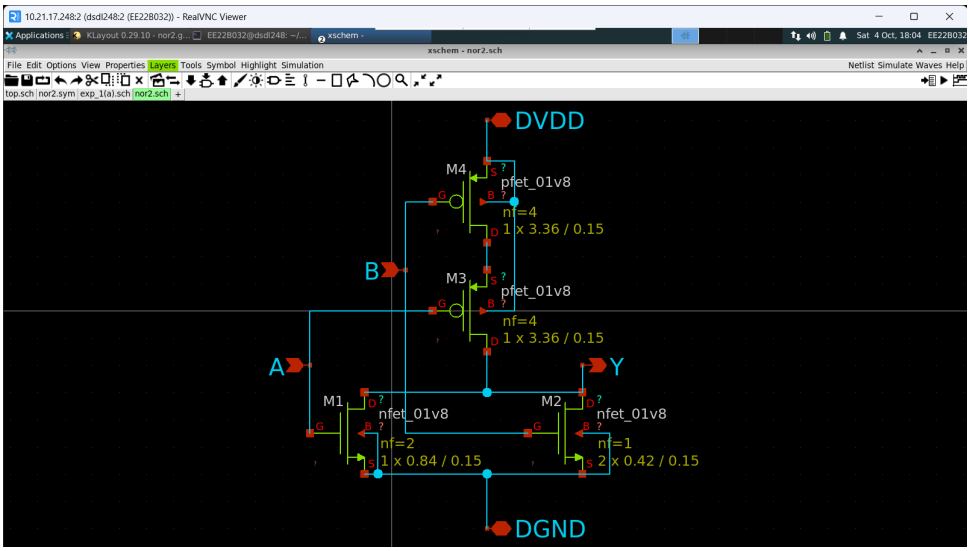


Schematic

Testbench

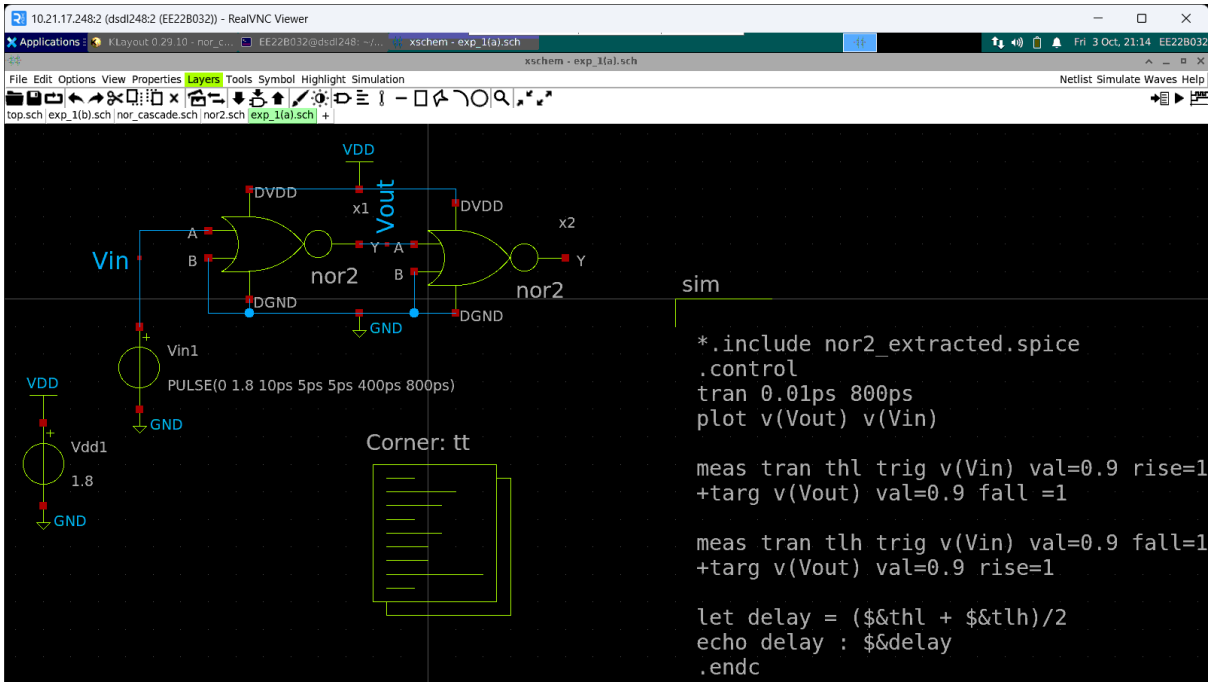


Without Parasitics

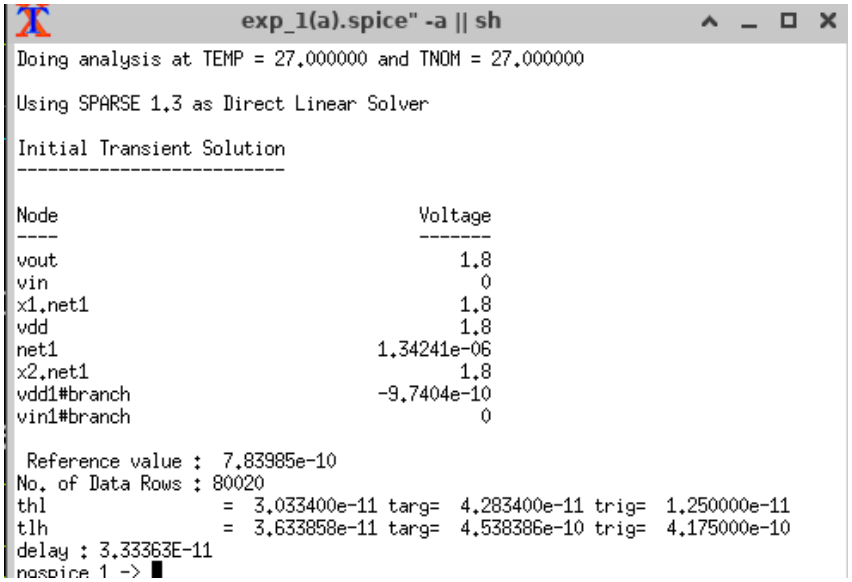


Delay

With Parasitics

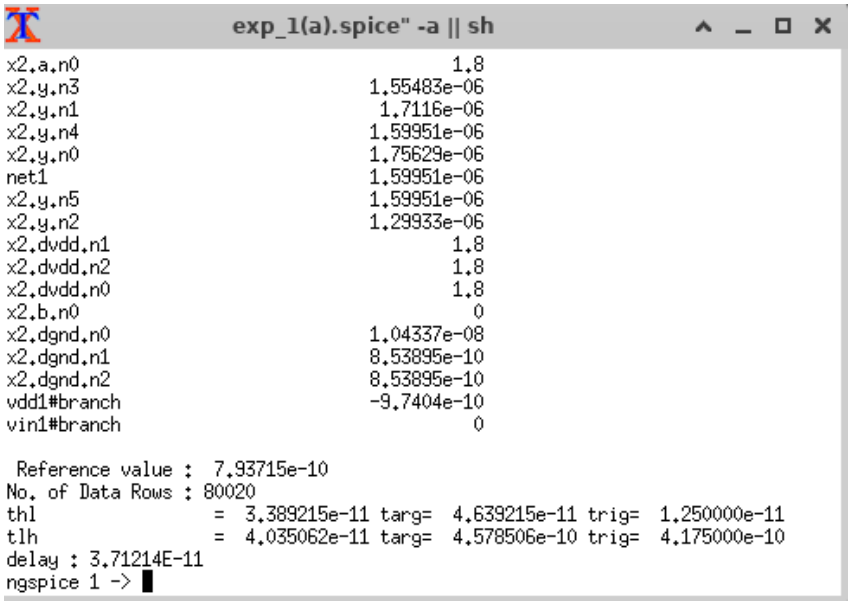


Delay

Analytical

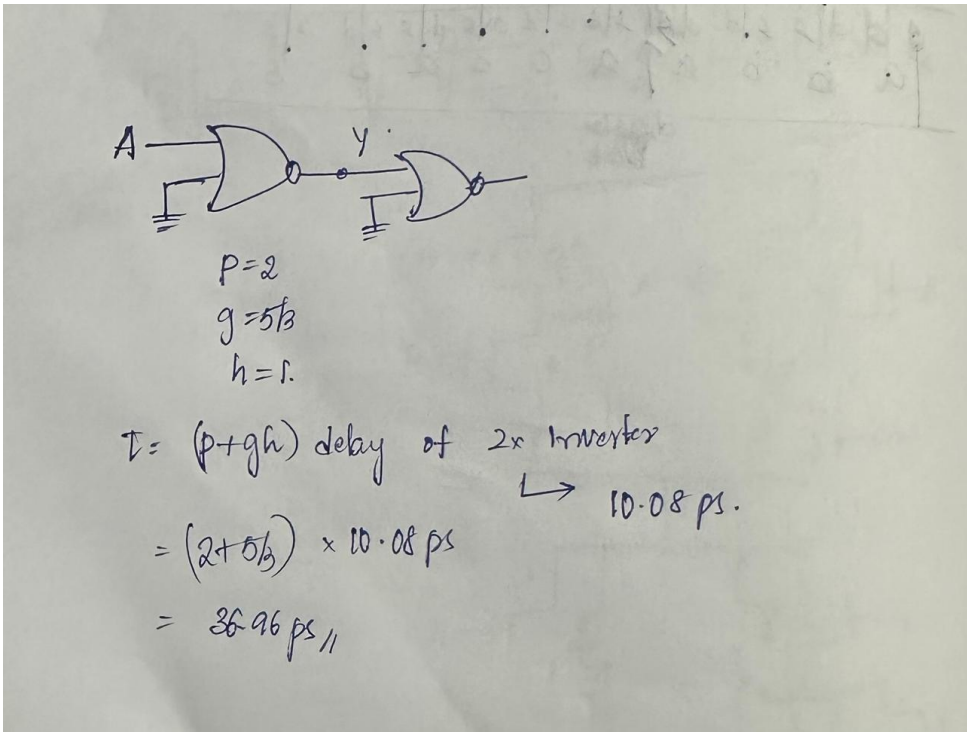


Analytical

Part B

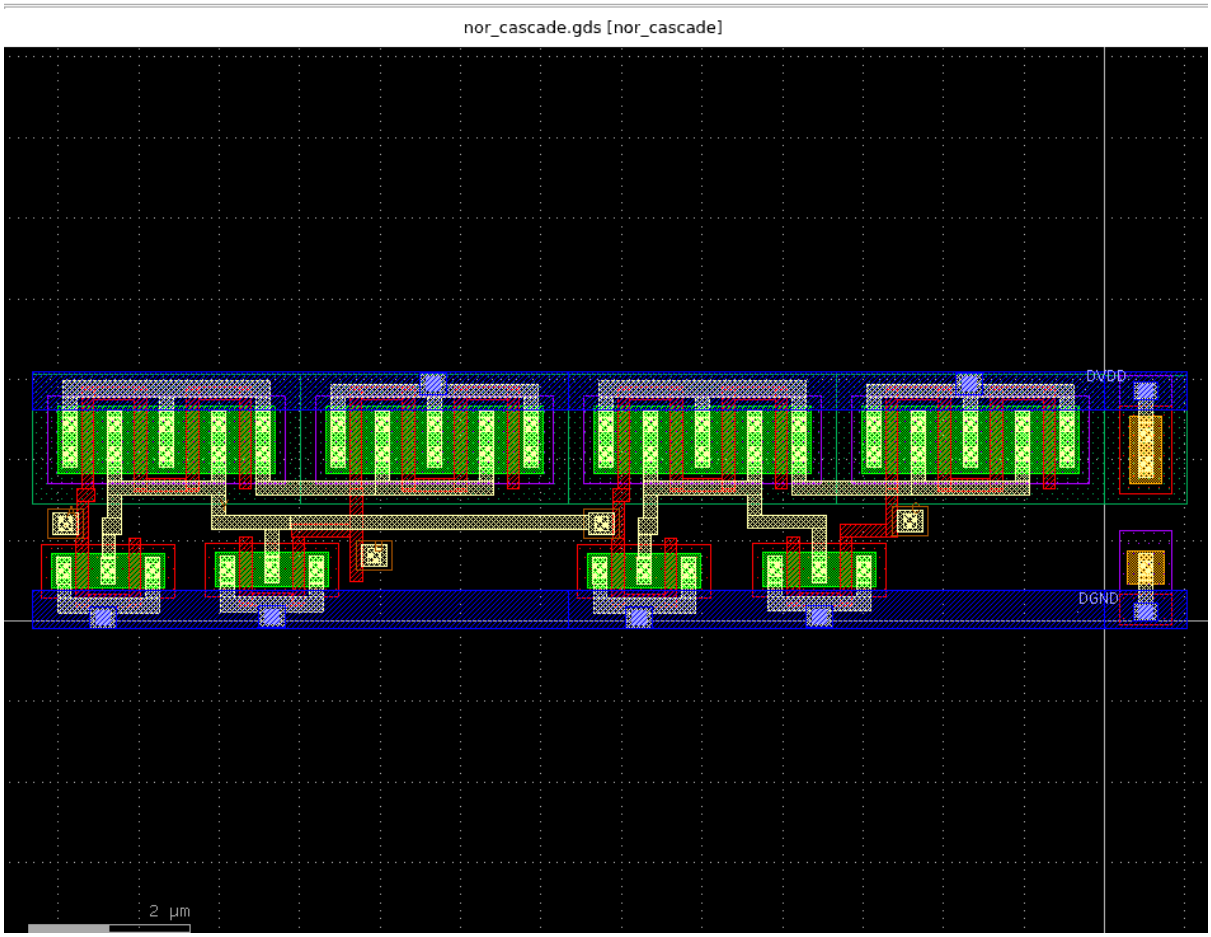


Schematic

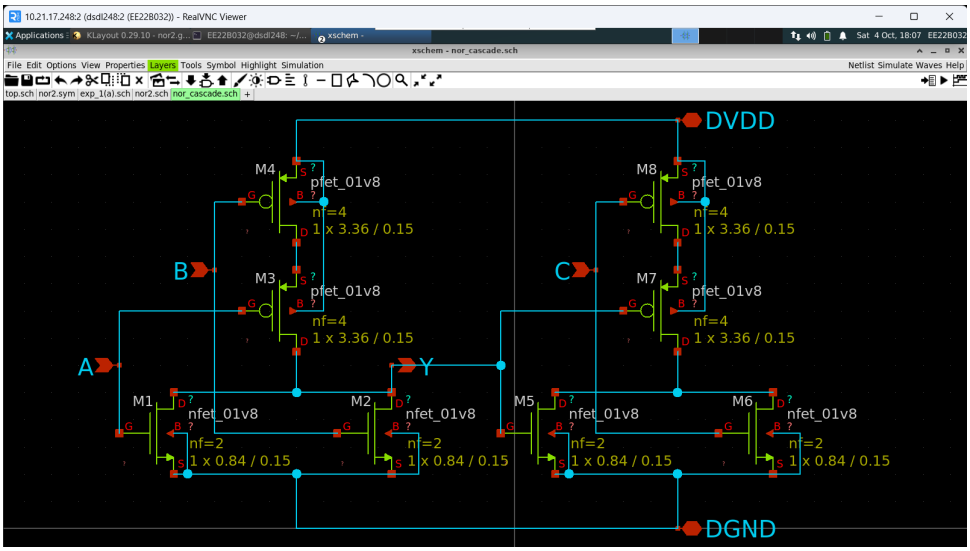


Schematic

Testbench

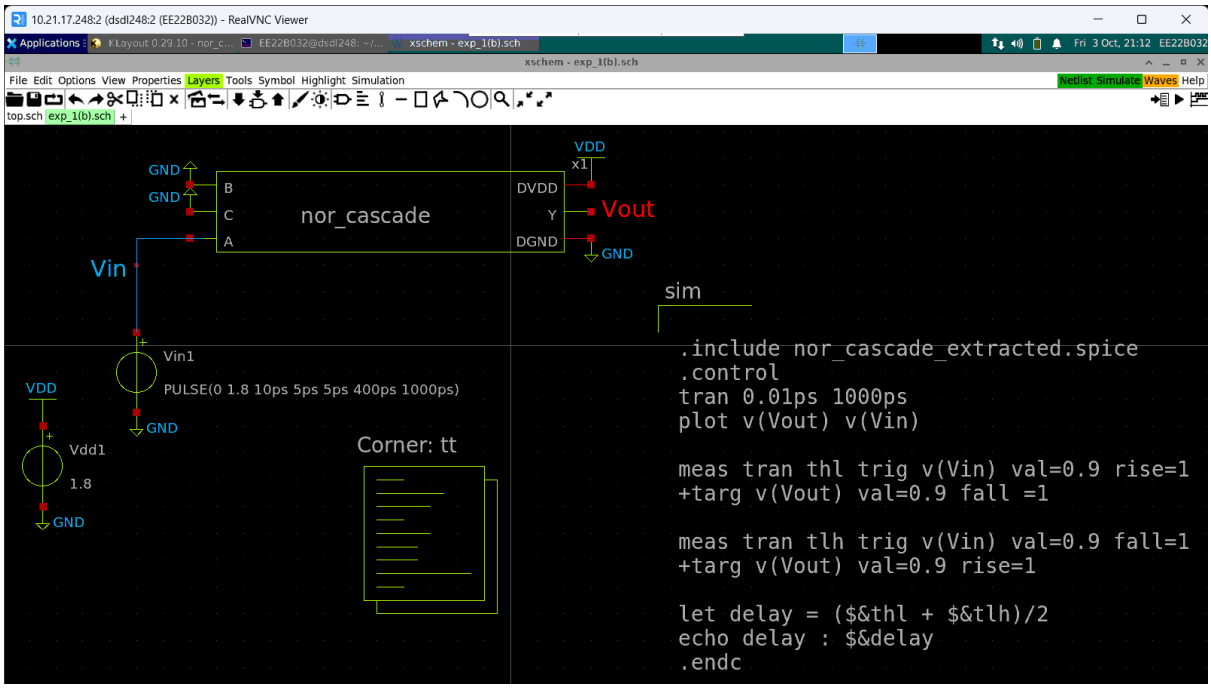


Without Parasitics

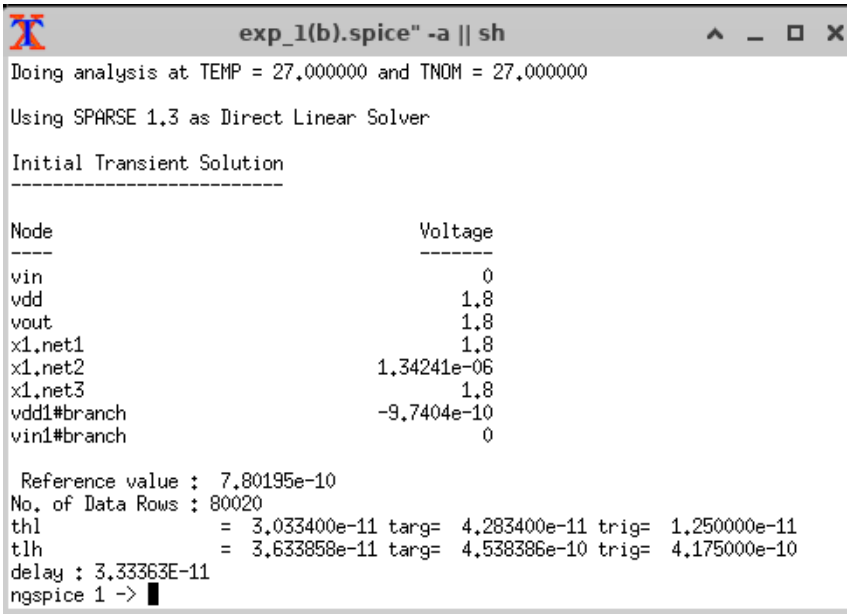

Delay

With Parasitics

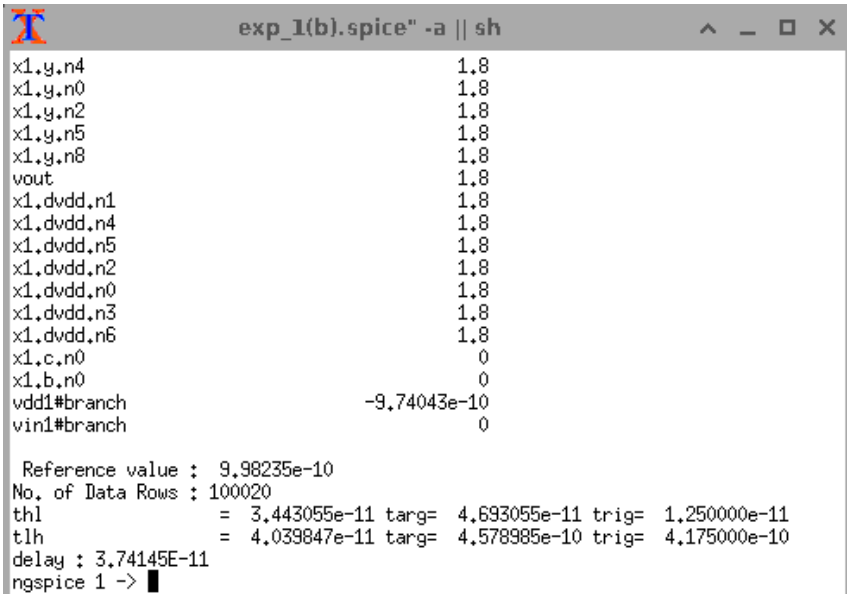

Delay